

tipo de corriente


Circuito

Gráfico onda

Ecuaciones

*cc = corriente continua

CA

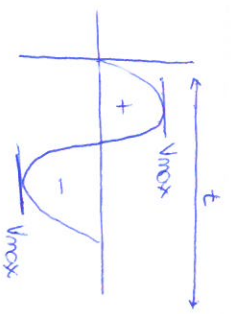


$$V_{ef} = \frac{V_{max}}{2}$$

$$V_{cc} = 0 \text{ v. (lo que suma = lo que resta)}$$

$$V_{pp} = 2 \cdot V_{max}$$

CA

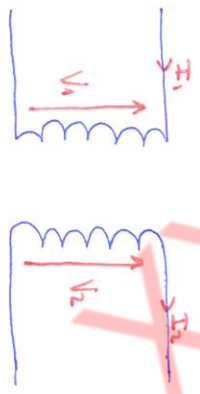

$$m = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$


(transformador ideal)

$$ef = \frac{1}{2} \text{ o } \frac{1}{\sqrt{2}}$$

↑ medio
↓ 2 veces

CC

Media onda

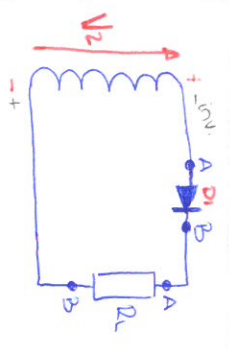

$$V_{aef} = \frac{V_{max}}{2}$$

$$V_{a_{cc}} = \frac{1 \cdot V_{max}}{\pi}$$

$$V_{D1_{min}} = V_{AB} \text{ diodo invertido } +$$

$$I_{D1_{ef}} = \frac{I_{a_{max}}}{2}$$

$$I_{D1_{cc}} = \frac{1 \cdot I_{a_{max}}}{\pi}$$

$$I_{a_{max}} = \frac{V_{a_{cc}}}{R_L}$$

$$V_{D1_{min}} = V_{AB} \text{ diodo } -$$



$$f = \frac{1}{T}$$

$$f_{alida} = 1 \cdot f_{entradado}$$

$$I_{a_{max}} = \frac{V_{a_{cc}}}{R_L}$$

CC

onda completa

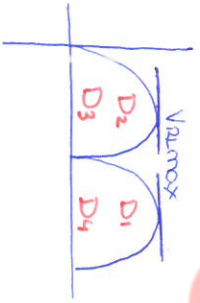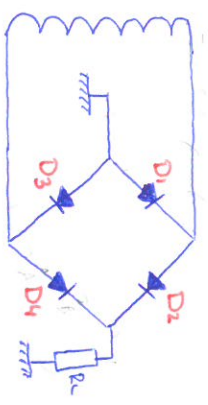

$$V_{aef} = \frac{V_{max}}{\sqrt{2}}$$

$$V_{a_{cc}} = \frac{2 \cdot V_{max}}{\pi}$$

$$V_{D1_{min}} = V_{max} - 1 \frac{1}{4} \text{ silicio}$$

$$I_{D1_{ef}} = \frac{I_{a_{max}}}{2}$$

$$I_{D1_{cc}} = \frac{1 \cdot I_{a_{max}}}{\pi}$$



$$I_{a_{max}} = \frac{V_{a_{cc}}}{R_L}$$

$$V_{D1_{min}} = V_{AB} \text{ diodo } -$$

$$f_{alida} = 2 \cdot f_{entradado}$$

CC

onda onda

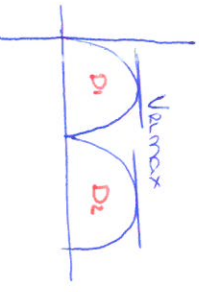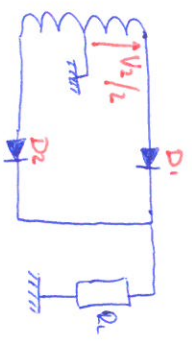

$$V_{a_{max}} = \frac{V_{2_{max}}}{2} - 0 \text{ v. silicio}$$

$$I_{a_{max}} = \frac{V_{a_{max}}}{R_L}$$

*El resto de formulas son iguales